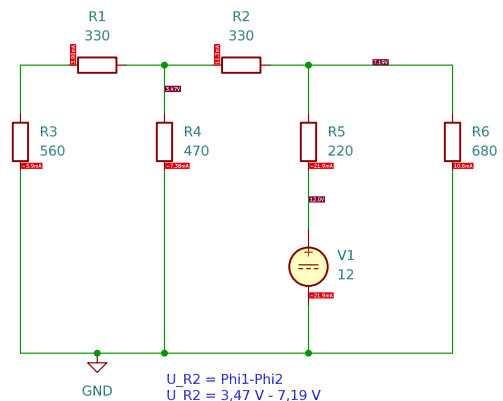




$U_{R2} = \Phi_{i1} - \Phi_{i2}$
 $U_{R2} = 3,47 \text{ V} - 7,19 \text{ V}$
 $U_{R2} = -3,72 \text{ V}$
 $11,3 \text{ mA} * 330 \text{ Ohm} = 3,729 \text{ V}$